

EEL2020 Digital Design Lab Report

Sem II AY 2023-24

| | | |
|---------------------------------|---|---------------------------|
| Experiment No. | : | 07 |
| Name | : | Lavangi Parihar |
| Roll No. | : | B22EE044 |
| Partner Name (Partner Roll No.) | : | Chaital V Ghan (B22CS020) |

Objective

- (a) Designing a 4-bit shift Register
- (b) Multiplier using shifter and adder

4-BIT SHIFT REGISTER

Logic Design

It takes a 4-bit input and extends it to a 6-bit output by appending two zeros at the beginning. This effectively creates a 4-bit shift register where the input is shifted by two positions to the right, and the vacated positions are filled with zeros.

Source Description

- Design source

```
module extend_input(  
    input [3:0] in, // 4-bit input  
    output [5:0] out // 6-bit output  
);
```

```
// Prepend two '0's to the 4-bit input to make it a 6-bit output  
assign out = {2'b00, in};
```

```
endmodule
```

- Simulation source (if any)

```
`timescale 1ns / 1ps
```

```
module extend_input_tb;
```

```
    // Testbench signals  
    reg [3:0] in;  
    wire [5:0] out;
```

```

// Instantiate the module under test
extend_input dut(
    .in(in),
    .out(out)
);

initial begin
    // Initialize input
    in = 4'd0; // Start with 0

    // Apply different inputs and wait 10 time units between each
    #10 in = 4'd1; // 1
    #10 in = 4'd2; // 2
    #10 in = 4'd3; // 3
    #10 in = 4'd4; // 4
    #10 in = 4'd5; // 5
    #10 in = 4'd6; // 6
    #10 in = 4'd7; // 7
    #10 in = 4'd8; // 8
    #10 in = 4'd9; // 9
    #10 in = 4'd10; // 10
    #10 in = 4'd11; // 11
    #10 in = 4'd12; // 12
    #10 in = 4'd13; // 13
    #10 in = 4'd14; // 14
    #10 in = 4'd15; // 15

    #10 $finish; // End simulation
end

// Monitor changes and print
initial begin
    $monitor("Time = %t, Input = %4b, Output = %6b", $time, in, out);
end


Endmodule

```


Video Implementation:

[Link](#)

Simulation Results (Timing diagram)

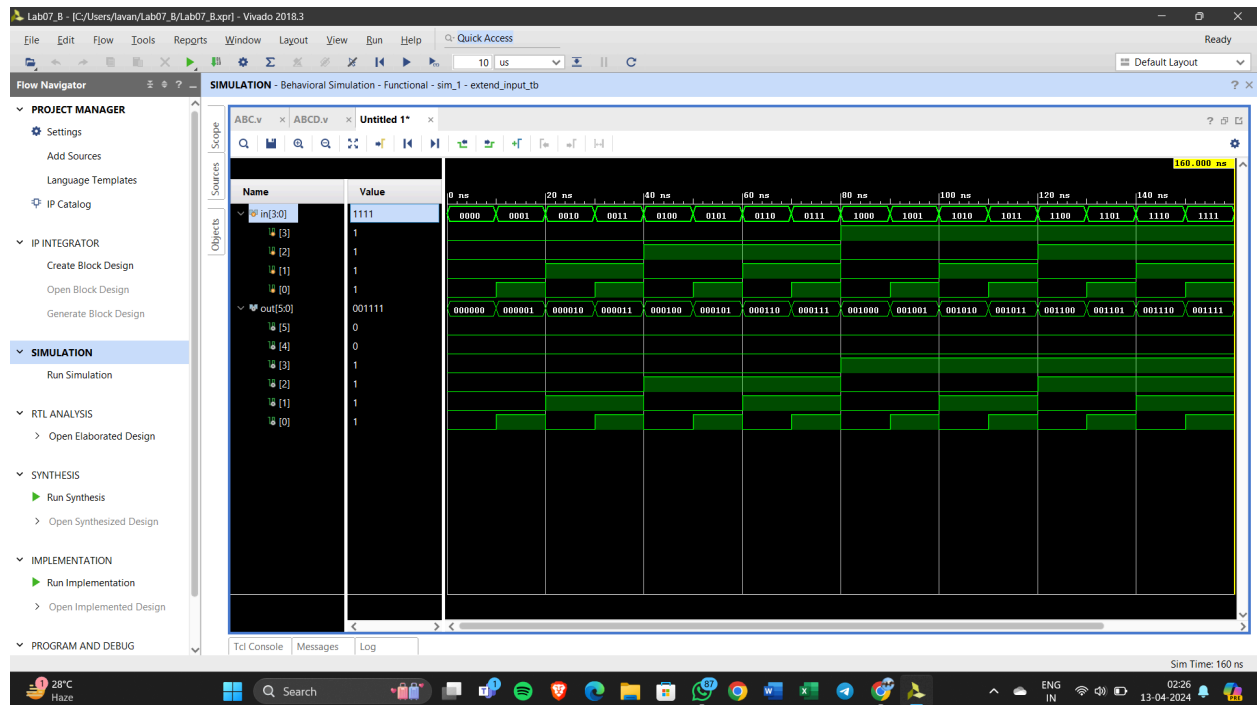


Elaborated Design

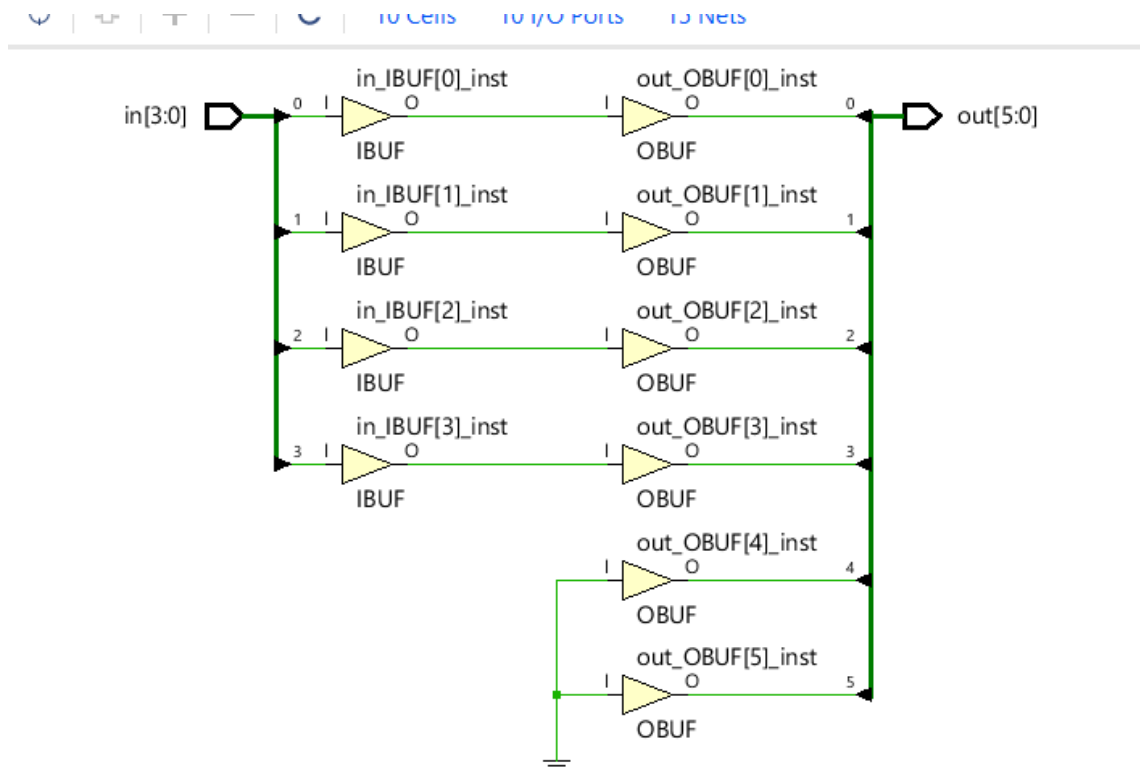

MULTIPLIER USING SHIFTER AND ADDER

Logic Design

 It takes a 4-bit input and multiplies it by 6 by first multiplying it by 2 (shifting left by 1) and then by 4 (shifting left by 2), and finally adding the two shifted values together.



Source Description

- Design source

```
module six_multiplier(  
    input [3:0] in, // 4-bit input  
    output [6:0] out // 7-bit output  
);  
    // Intermediate values for shifted inputs  
    wire [4:0] shift_one;  
    wire [5:0] shift_two;  
  
    // Shift operations  
    assign shift_one = in << 1; // Multiply by 2  
    assign shift_two = in << 2; // Multiply by 4  
  
    // Sum the two shifted values  
    // Since shift_one is 5 bits and shift_two is 6 bits,  
    // we need to align them for addition.  
    // We will use a 6-bit representation for shift_one_sum to align with shift_two.  
    wire [5:0] shift_one_sum = {1'b0, shift_one}; // Prepend a 0 to make it 6 bits  
    assign out = shift_one_sum + shift_two; // The sum will be a 7-bit number  
  
Endmodule
```

- Simulation source (if any)

```
`timescale 1ns / 1ps  
  
module six_multiplier_tb;  
  
    // Testbench signals  
    reg [3:0] in;
```

```

wire [6:0] out;

// Instantiate the design under test
six_multiplier dut(
    .in(in),
    .out(out)
);

initial begin
    // Initialize input
    in = 4'd0;

    // Apply different inputs and wait 10 time units between each
    #10 in = 4'd1;
    #10 in = 4'd2;
    #10 in = 4'd3;
    #10 in = 4'd4;
    #10 in = 4'd5;
    #10 in = 4'd6;
    #10 in = 4'd7;
    #10 in = 4'd8;
    #10 in = 4'd9;
    #10 in = 4'd10;
    #10 in = 4'd11;
    #10 in = 4'd12;
    #10 in = 4'd13;
    #10 in = 4'd14;
    #10 in = 4'd15;

    #10 $finish; // End simulation
end

// Monitor changes and print
initial begin
    $monitor("Time = %t, Input = %b, Output = %b", $time, in, out);
end


Endmodule

```

Video Implementation:

[Link](#)

Simulation Results (Timing diagram)

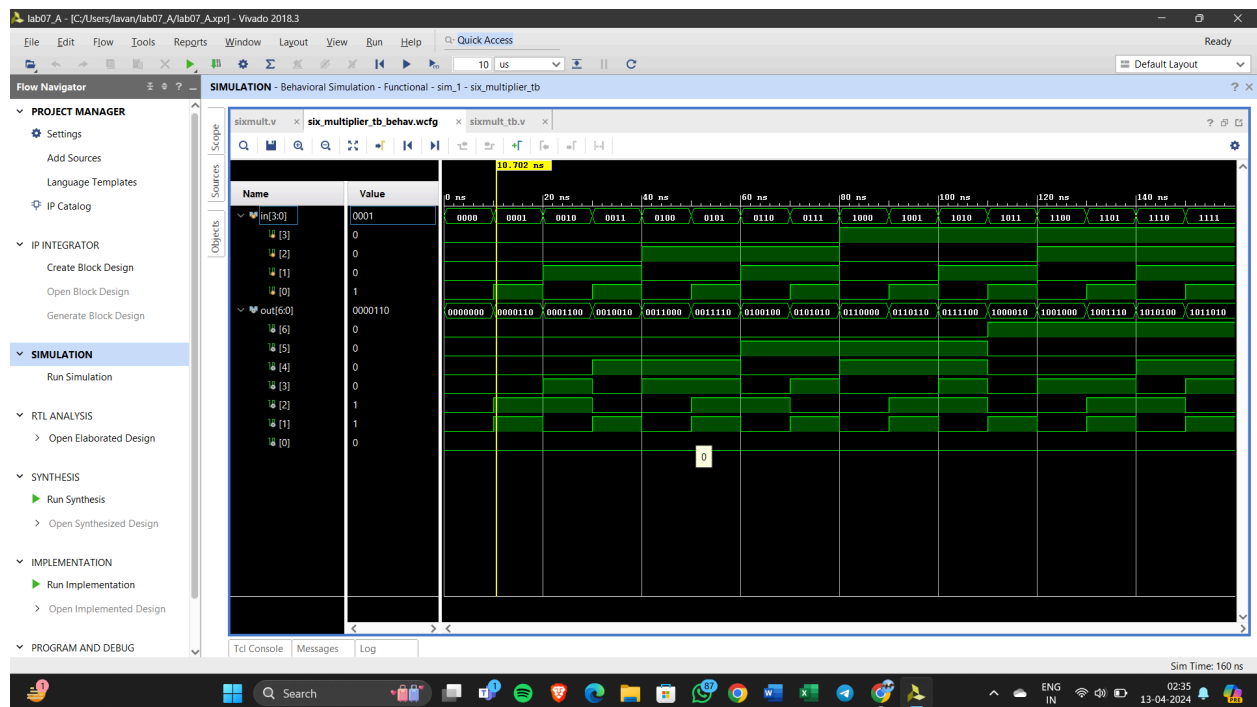

Elaborated Design

