

## Experiment 05

### Objectives

- (i) Design and simulate a  $4 \times 16$  decoder using  $2 \times 4$  decoders (with Enable)
- (ii) Design, simulate, and implement a Priority Encoder
- (iii) Design, simulate, and implement a Binary-to-Gray Code Converter

### (i) Decoder $4 \times 16$

A  $4 \times 16$  decoder can be made using five  $2 \times 4$  decoders as shown in Fig. 1.

 


Figure 1 Creating a  $4 \times 16$  decoder using  $2 \times 4$  decoders with enable

### Procedure

**Step 1:** Write a Verilog module for a  $2 \times 4$  decoder, and use it to create a  $4 \times 16$  decoder as shown in Fig. 1.

**Step 2:** Write a testbench to simulate the results for at least eight inputs combinations. Verify the timing diagram with the truth table, **and save the screenshot for the report.**

## Experiment 05

### Code Converters

**Step 3:** Use the four slide switches on the RPI module as inputs (eg. Inputs ( $I_0$   $I_1$   $I_2$   $I_3$ ) on Switches ( $H$   $G$   $F$   $E$ )). To display the sixteen distinct decoder outputs, use 06 LEDs on the RPI module (eg.  $D_0 - D_5$ ), 04 on the PYNQ-Z2 board (eg.  $D_6 - D_9$ ). The remaining six can be shown as R-G-B combinations on the two RGB LEDs or by connecting six external LEDs to the PMod. **Update the same on the RPI and PYNQ Z2 XDC files (and include the updates in your report).**

**Step 2:** Generate bitstream and program the device. Verify the working of all combinations of inputs.

**Record a video showing all input/output combinations.**

 


Figure 2 Circuit Schematic of the connections

### (ii) 4-bit Priority Encoder

A Priority Encoder implements a priority function: If more than one inputs are 1, the input having highest priority takes precedence. Here, the input having higher index will take priority.

(V shows Valid priority;  $V = 1$  only when at least one of the priority inputs are high). The Truth Table is shown in Table 1.

#### Procedure

**Step 1:** Write the Verilog module for the priority encoder based on the Truth Table (Table 1). Simulate the circuit with a testbench showing at least 8 input combinations. (Insert the timing diagram in your report).

## Experiment 05

### Code Converters

**Step 2:** Refer to Figure 3 for connections and input/output configurations. Update the XDC files and insert the updates in your report.

**Step 3:** Generate the bitstream and program the device. Verify all input combinations and record a video for your demonstration.

**Table 1 Truth Table of a 4-bit Priority Encoder**

Inputs				Outputs		
$I_0$	$I_1$	$I_2$	$I_3$	$Y$		$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

 



Figure 3 Connections and input/output pin configurations

### (iii) 4-bit Binary-to-Gray Converter

A 4-bit Binary-to-Gray converter takes a 4-bit binary number and converts it to corresponding Gray code. Refer to the truth table and the logic circuit shown in Table 2

**Table 2 Truth Table for Binary-to-Gray Decoder**

$B_3$	$B_2$	$B_1$	$B_0$	$G_3$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

 

**Figure 4** Logic circuit of Binary-to-Gray Converter

### Procedure

**Step 1:** Write the Verilog module for the Binary-to-Gray Converter.

**Step 2:** Create a testbench and simulate at least eight combinations. Save the timing diagram for your report.

**Step 3:** Update the XDC files of RPI module and PYNQ Z2 boards as follows:

Input ( $B_3 B_2 B_1 B_0$ ) – RPI Switches ( $H, G, F, E$ ) respectively

## Experiment 05

### Code Converters

Output ( $G_3 G_2 G_1 G_0$ ) – PYNQ Board LEDs (LD3, LD2, LD1, LD0) respectively.

**Step 4:** Generate the bitstream, program the device. Verify all input-output combinations and record a video showing at least ten combinations.

### Online Reference

R. Chouhan, *Experiment 05, EEL2020 Digital Design* ([Lab Notes](#))

---